

# Modified SEPIC converter fed motor drive using ANN controller

## Jaipriya P<sup>1</sup>, Geetha V<sup>2</sup>

<sup>1</sup>Jaipriya P PG scholar, power electronics and drives ,Government college of Engineering, Salem. <sup>2</sup>Geetha V Professor & HOD EEE, Government college of Engineering, Salem. <sup>3</sup>Third Author Department & College

**Abstract** - Modern day-to-day devices also use an AC sourceas an input while working with DC voltage. An AC-DC converter is used to get an effective and versatile DC output. Without sacrificing conversion efficiency, however, traditional converters are not suitable for high voltage output. Within this paper a new topology called the Cascaded Boost-SEPIC (CBS) converter is suggested. The converter is validated on the basis of conversion efficiency, minimum THD and maximum power factor. The results obtained evinces the improvement achieved in the power quality.

\*\*\*

*Key Words*: AC-DC Converter; ANN (Artificial Neural Network controller); Separately excited DC motor

#### **1.INTRODUCTION**

Electronic devices are used in grid-connected systems, communication systems, and power supply systems etc. which play an indispensable role in our daily lives. Devices operate in variable voltage levels. A converter that facilitates the capability of different level of operating voltage is essential for versatile use. But not all converters are able to make conversion properly without compromising performance. It is almost always the case that a tradeoff has to be made between necessity and performance. High voltage gain will cause for a deterioration of signal shape (high THD).

The overall efficiency goes down slightly as the duty cycle rises in conventional converter. <sup>[1][8]</sup> Again increasing duty cycle causes conduction losses and serious reverse-recovery problem in diodes. <sup>[9][10]</sup> Also Boost converter can operate with lower voltage level of MOSFET. Boost converter also gives output with lower distortion which makes the circuit manage the THD level as low as possible.


In this paper a new topology is introduced – Cascaded Boost SEPIC (CBS), which is used to avail different voltage level in accordance the duty cycle. Higher voltage conversion can be achieved using cascaded Boost-SEPIC converter.

#### 1. Block diagram

The following block diagram that consist of AC supply that is rectified by the full wave rectifier and converted into DC supply and then the switch is controlled by the ANN controller and given to the motor load.


\_\_\_\_\_

#### **Block diagram**

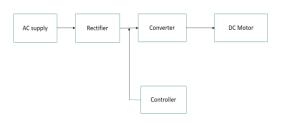
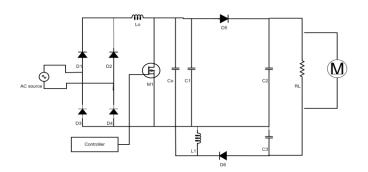
#### **Circuit diagram**

In this Fig 3.1.1 it shows that the circuit diagram of the SEPIC converter with given input AC supply to the circuit and the diode it converts into DC supply by using the full bridge rectifier and then the switch is being controlled by using ANN (Artificial Neural Network) and then output will given to the load.




I



### Modes of operation

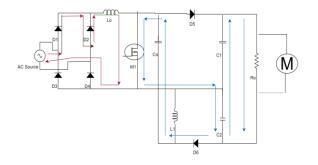
#### Mode 1:

In mode 1 operation Fig 3.2.1 shows that the current flows from the higher potential to the lower potential. At mode 1 when the switch is ON, the diode  $D_5$  will not conduct and the current flows from the supply through diode  $D_6$  and  $C_2$  supplies energy to load.



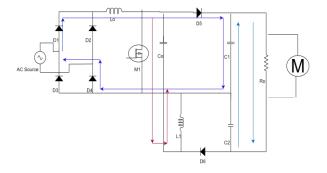
## Mode 2:

In mode 1 operation Fig 3.2.2 shows that the current flows from the higher potential to the lower potential. At mode 2 when the switch is OFF, the diode  $D_6$  will not conduct and the current flows from the supply through diode  $D_5$  and  $C_3$  supplies energy to load.




#### Mode 3:

In mode 3 operation Fig 3.2.3 shows that the current flows from the lower potential to the higher potential. At mode 3 when the switch is ON, the diode  $D_5$  will not conduct and the current flows from the supply through diode  $D_6$  and  $C_2$  supplies energy to load.

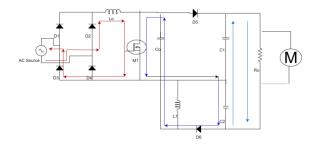

Mode 4:

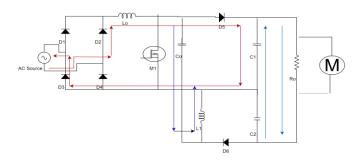In mode 4 operation Fig 3.2.4 shows that the current flows from the lower potential to the higher potential. At mode 3 when the switch is OFF, the diode  $D_6$  will not conduct and the current flows from the supply through diode  $D_5$  and  $C_3$  supplies energy to load.



#### Table of modes of operation:

Modes	Switch	Conduction of	Energy
		diode	flow
Mode 1(Higher			
potentialto	ON	$D_6$	$C_2$
lower)			
Mode 2Low to			
high potential	OFF	$D_5$	$C_3$
Mode 3(Higher			
potential to	ON	$D_6$	$C_2$
lower			
potential)			
Mode 4(Low to			
high potential)	OFF	$D_5$	C <sub>3</sub>

I



#### Modelling of the Converter

The voltage gain of the converter is calculated by the given formula.

$$v_0 = v_{01} + v_{02}$$

$$v_0 = \frac{1}{(1-D)}v_i + \frac{D}{(1-D)}v_i$$
 ----- <sup>2</sup>

$$v_0 = Gv_i$$

$$G = \frac{(1+D)}{(1-D)}$$
 ------3

Design of the converter

#### **Selection of Inductor**

$$\Delta I_L = I_N \times 40\% = I_{out} \times \frac{v_{out}}{v_{in}} \times 40\%$$

Where  $\Delta I_L$  = Ripple current of inductors

I<sub>N</sub> =Input current

I<sub>out</sub> = Output current

$$L_o = L_1 = L - \frac{v_{in(min)}}{\Delta I_L \times fsw}$$

## **Selection of Capacitor**

$$I_{out(RMS)} = I_{out} \times \sqrt{\frac{v_{out} + v_D}{Vin \ min}}$$

Iout = Output current

$$C_{out} \geq I_{out} \times \frac{I_{ou}t \times D}{V_{ripple} \times 0.5}$$

C<sub>out</sub> is the output capacitance

## **Selection of Diode**

$$VRD1 = VIN (max) + VOUT (max)$$

Minimum peak reverse voltage the diode must withstand is  $=\!V_{\text{RD1}}$ 

## **Simulation Diagram**

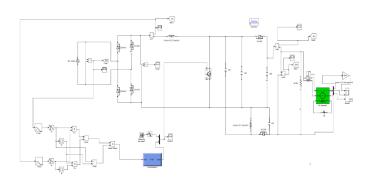


Fig 1.1 Simulation diagram

## **Simulation Results**

## Input Voltage waveform

Fig 1,2 Shows the input voltage waveform that is obtained in the MATLAB/SIMULINK.

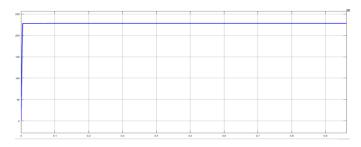


Fig 1.2 Input voltage waveform

## **Input Current Waveform**

Fig 1.3 Shows the simulated waveform of input current in MATLAB/ SIMULINK.

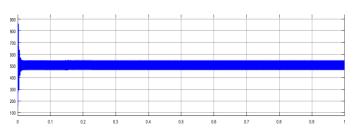


Fig 1.3 Input current waveform.

I



## Input voltage after rectification

Fig 1.4 Shows the simulated waveform of the input voltage after rectification in MATLAB/SIMULINK.

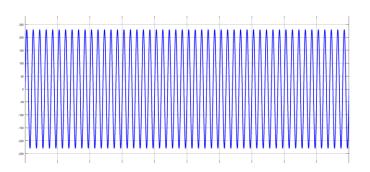


Fig 1.4 Input voltage rectification

## **Output current waveform**

Fig 1.5 Shows the waveform of the output current that is simulated in MATLAB/ SIMULINK.

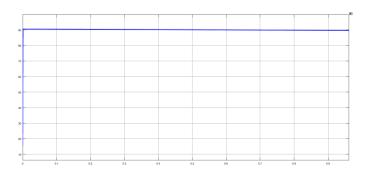


Fig 1.5 Output current waveform

## **Output voltage Waveform**

Fig 1.5 Shows the waveform of the output current that is simulated in MATLAB/ SIMULINK.

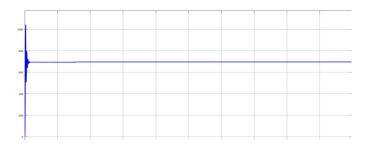


Fig 1.6 output voltage waveform

## **Simulated Parameters**

Table 1.1 Shows the simulated parameters

Parameters	Values
Input voltage	230V
$L_0$ , $L_1$	3.36µH
$C_0$ , $C_1$	4.7µF
C <sub>2</sub> , C <sub>3</sub>	100µF

## **3. CONCLUSIONS**

The proposed MBS converter designed by cascading Boost and SEPIC converter to obtain the advantages of both the converters. The maximum efficiency the circuit can produce without any controller is 97.8%. However the THD was quite high which is brought down to 9.94% by using the PI controller. The power factor is also improved with the addition of the PI controller. The proposed MBS converter can be effectively used for high voltage DC application like DC micro grid, heater etc.

## REFERENCES

[1]Wilmar Martinez, Camilo A. Cortes, Jun Imaoka, Kazuhiro Umetani, Masayoshi Yamamoto, "Current ripple modeling of an interleaved high step-up converter with coupled inductor", Future Energy Electronics Conference and ECCE Asia (IFEEC 2017 -ECCE Asia) 2017 IEEE 3rd International, pp. 1084-1089, 2017.

[2] Y. Liang, "A New Type of Statcom Based on Cascading Voltage Source Inverters with Phase-shitted Unipolar SPWM", IAS'98

[3] D.-H. Lee, F. C. Lee, "New Cascade Switch Multilevel PWM Converters", APEC'99, pp. 329-324.

[4] L. Huber, M. M. Jovanovic, "A design approach for server power supplies for networking applications", Proc. 15th Annu. IEEE Appl. Power Electron. Conf. Exp., pp. 1163-1169, 2000.

[5] L. Muller, J. W. Kimball, "High gain DC-DC converter based on the cockcroft-walton multiplier", IEEE Transactions on Power Electronics, vol. 31, no. 9, September 2016.

[6] J. P. de Souza, DE Oliveira, R. Gules, E. F. R. Romaneli, A. A. Badin, "A high static gain CUK DC-DC converter", IEEE 13th Brazilian Power Electronics



Conference and 1st Southern Power Electronics Conference, 2015.

[7] A. A. A. Freitas, F. L. Tofoli, E. M. Sa, S. Daher, F. L. M. Antunes, "High-voltage gain DC-DC boost converter with coupled inductors for photovoltaic systems", IET Power Electronics, vol. 8, no. 10, April 2015.

[8] R. W. Erickson, D. Maksimovic, Fundamentals of Power Electronics, Kluwer Academic Publishers, 2001.
[9] . Q. Zhao, F. Tao, F. C. Lee, P. Xu, J. Wei, "A simple and effective to alleviate the rectifier reverse-recovery problem in continuous-current-mode boost converter", IEEE Trans. Power Electron, vol. 16, no. 5, pp. 649-658, Sep. 2001.

[10] C. T. Pan, C. M. Lai, M. C. Cheng, L. T. Hsu, "A low switch voltage stress interleaved boost converter for power factor correction", IEEE Int. Conf. Power Electronics and Drive Systems, pp. 49-54, 2009.

L